



Specialization:	Electrical Engineering		Palestinian National Authority Ministry of Education & Higher Education Palestine Technical University College of Engineering & Technology Second Exam First semester 2010/2011	
Course Name:	Electrical Machine 1			
Date:	20/03/2011			
Time:	11:00-12:00			
Instructor:				
Name:		Section:	11 - 10	21 + 2/50

Notes: (Answer all questions)

د. انيس ابو سينا

23
50

Question #	1	2	3	4	Total Grade
Grade					

Q1) (15 points)

Choice the correct answer:

نعم الرفع بواسطة
م. مهن ابو عيسى

- The rotational losses of dc motors can be measured through:
 - ☒ no load test
 - ☐ blocked rotor test
 - ☐ full load test
- The mode of constant torque of dc motors occurs when :
 - ☐ increasing both armature voltage and field current
 - ☒ increasing the armature voltage and the flux remains unaffected
 - ☐ decreasing the flux at constant armature voltage
- Which one of the following motors will run away, if operated without load:
 - ☒ series dc motor
 - ☐ separately dc motor
 - ☐ compound dc motor
- In a dc generators, the voltage regulation measures
 - ☐ the shape of speed-torque characteristics
 - ☒ the shape of voltage-load current characteristics
 - ☐ the shape of voltage-field current characteristics
- Constant power mode of dc motor occurs when:
 - ☐ decreasing the flux and armature voltage increasing
 - ☒ increasing the armature voltage and the flux remains unaffected
 - ☐ decreasing the flux at constant armature voltage
- The basic of self-excitation of dc machines depends on an existing of
 - ☐ voltage of the field circuit
 - ☐ armature voltage
 - ☒ residual magnetism of the stator iron
 - ☐ residual magnetism of the rotor iron
- In series dc motors, the consumed current at 25 % loading is:
 - ☐ 3/4 of the rated current
 - ☒ 1/2 full rated current
 - ☐ 1/4 of the rated current
- Which one of the following motors is unsuitable for any application:
 - ☐ Series dc motor.
 - ☐ Cumulatively compound dc motor.
 - ☒ Differentially compound dc motor.
- Which one of the following machine is suitable for arc welding:
 - ☐ Series dc motor.
 - ☒ Series dc generator.
 - ☐ Differentially compound dc motor.
 - ☐ Differentially compound dc generator.
- The speed control of permanent-magnet (PM) dc motor is obtained through:
 - ☒ Armature voltage
 - ☐ field current
 - ☐ either (a) or (b)

$$P = T \omega$$

$$T = K \phi i_a$$


$$E_a = K \phi \omega$$

$$\omega = \frac{E_a}{K \phi}$$

$$P = K \phi i_a \times \frac{E_a}{K \phi}$$

$$P = i_a E_a$$

$$T = K \phi i_a$$

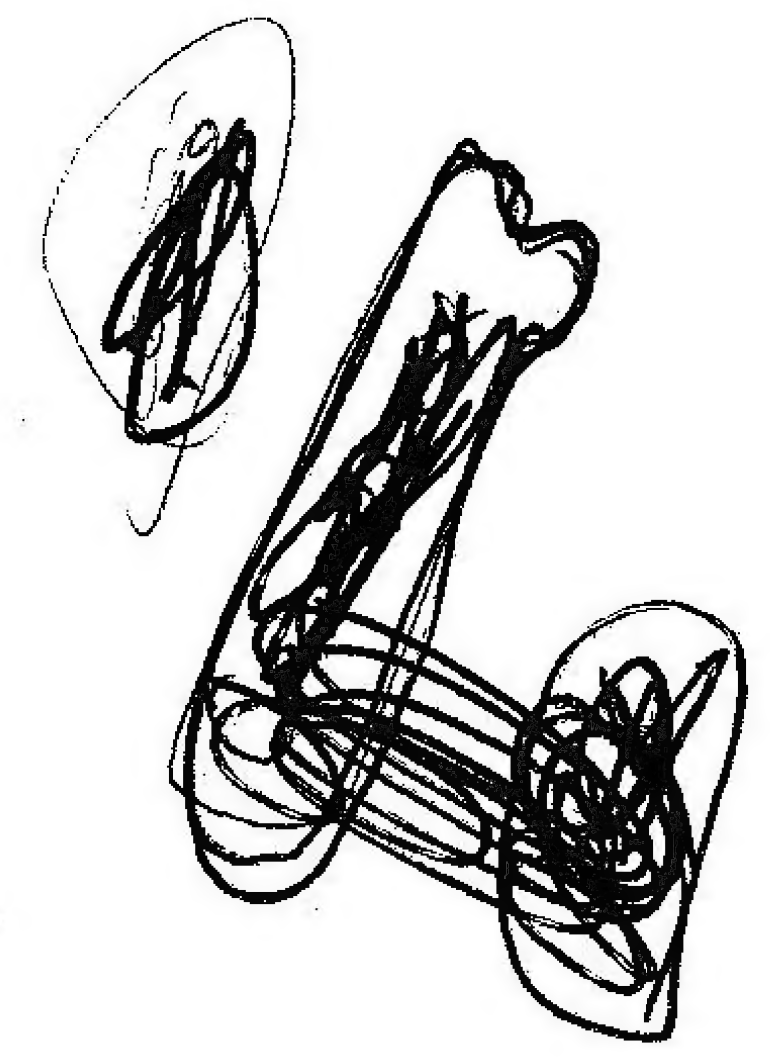

1

Q2) (14 points) (4)

A shunt DC generator is shown in Fig. 1. The shunt field resistor R_{adj} is adjusted to 180Ω , and the generator's rated speed is **1200 rpm**. Magnetization curve is shown in Fig. 2.

(a) What is the no-load terminal voltage of the generator at **1000 rpm**?

at no load $E_A = V_T$
 $I_F = \frac{V_T}{R_F + R_{adj}}$
 216

$n_2 = \frac{E_A}{E_{A0}} n_0$

$1000 = \frac{E_A}{E_{A0}} \times 1200$

$1000 = \frac{E_A}{240} \times 1200 \Rightarrow E_A = \frac{260000}{1200} = 216.6$

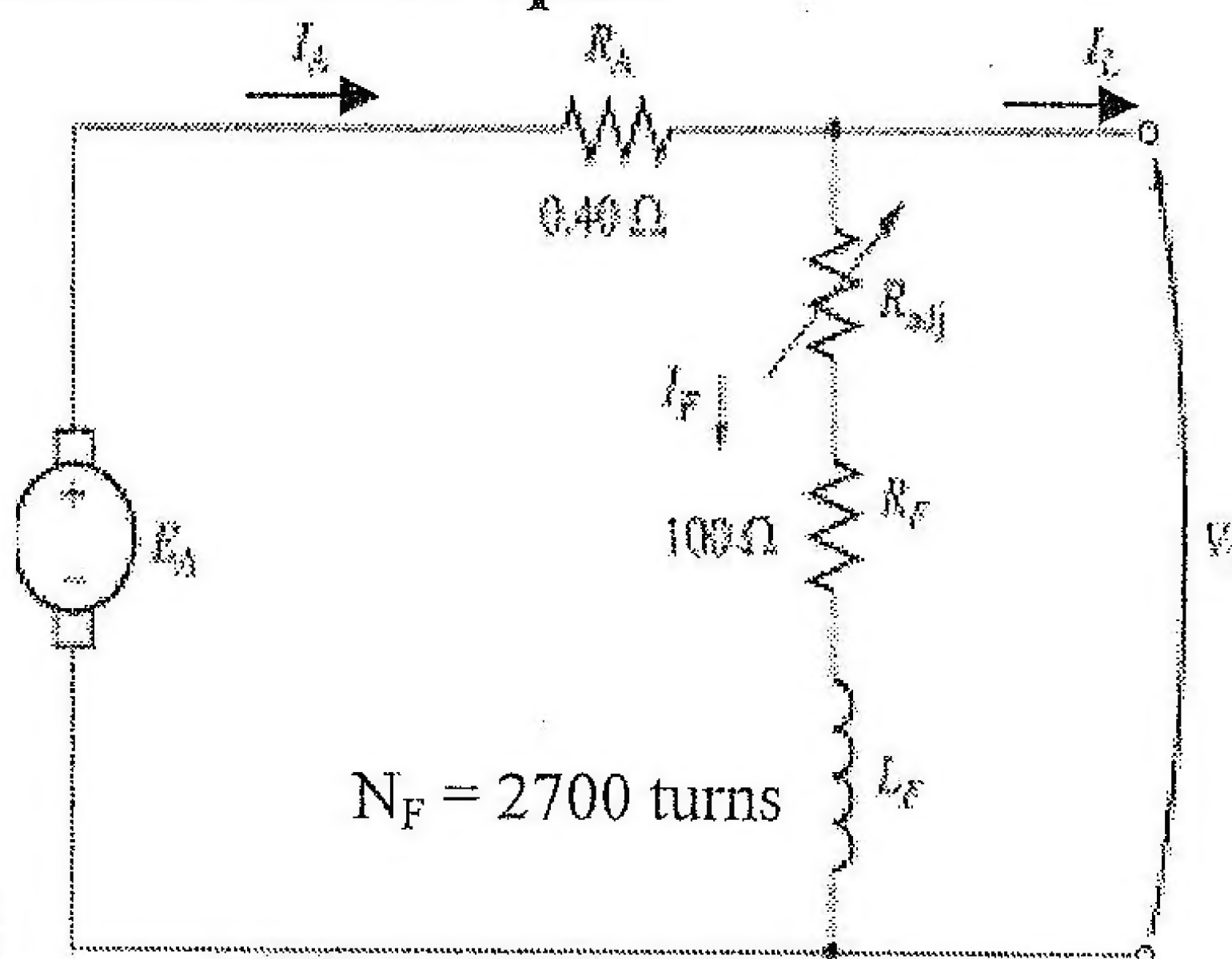


Fig. 1

(b) What is the terminal voltage of the generator at rated speed with an **armature current** of **100 A**?

$E_A = V_T - I_A R_A$
 $= 241.6 - 100(0.4)$
 $= 241.6 - 40$
 $= 201.6$
 $E_A \text{ at } 201.6$

$I_F = 0.48 \text{ A}$
 $n_2 = \frac{201.6}{241.6} \times 1200$

$n_2 = \frac{E_A}{E_0} n_0$

$E_A = \frac{n_2}{n_0} E_0$

$E_A = \frac{1001}{1200} \times 241.6$

$V_T = 201.6$


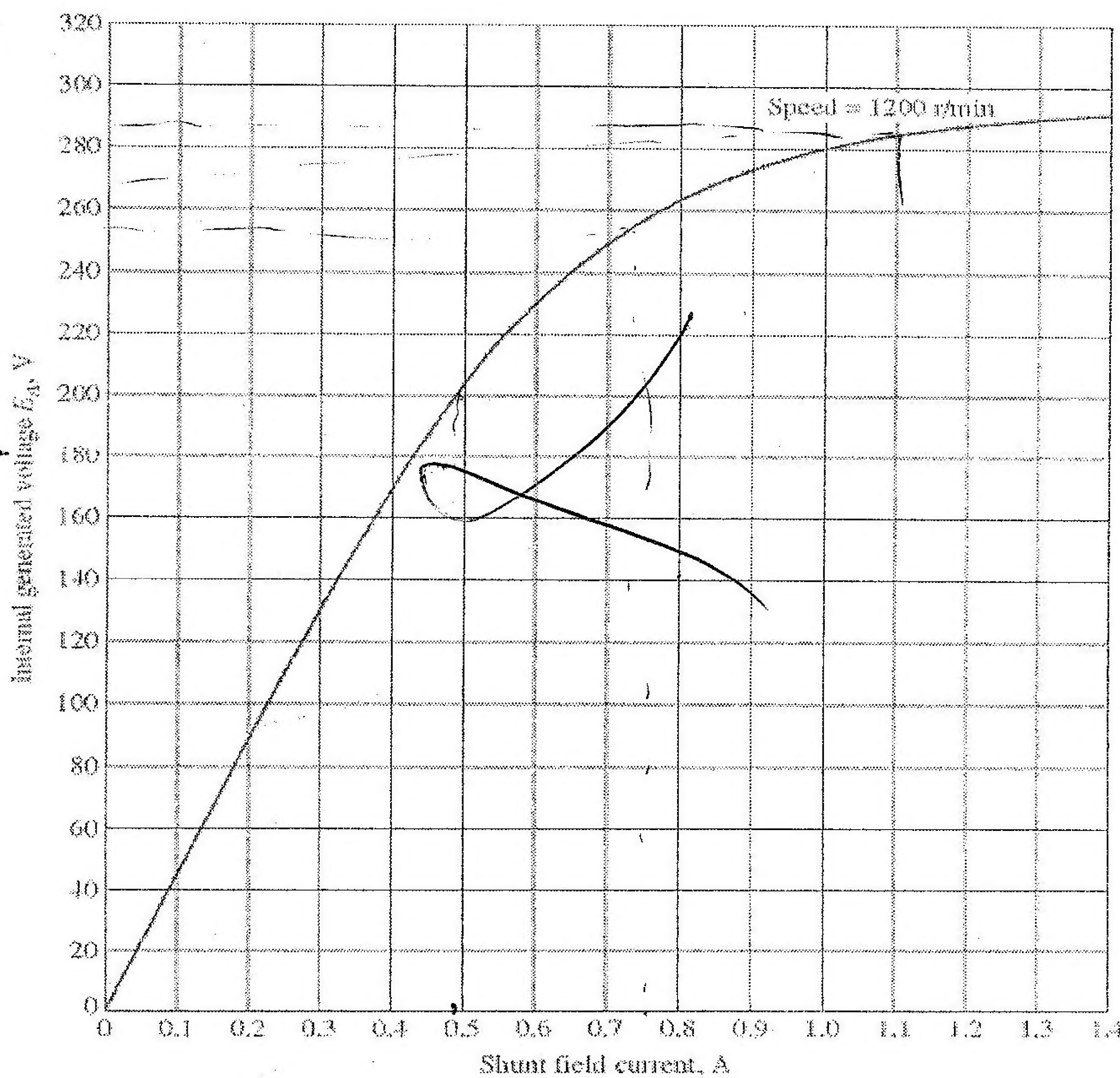



Fig. 2

Q3) (6 points) (2)

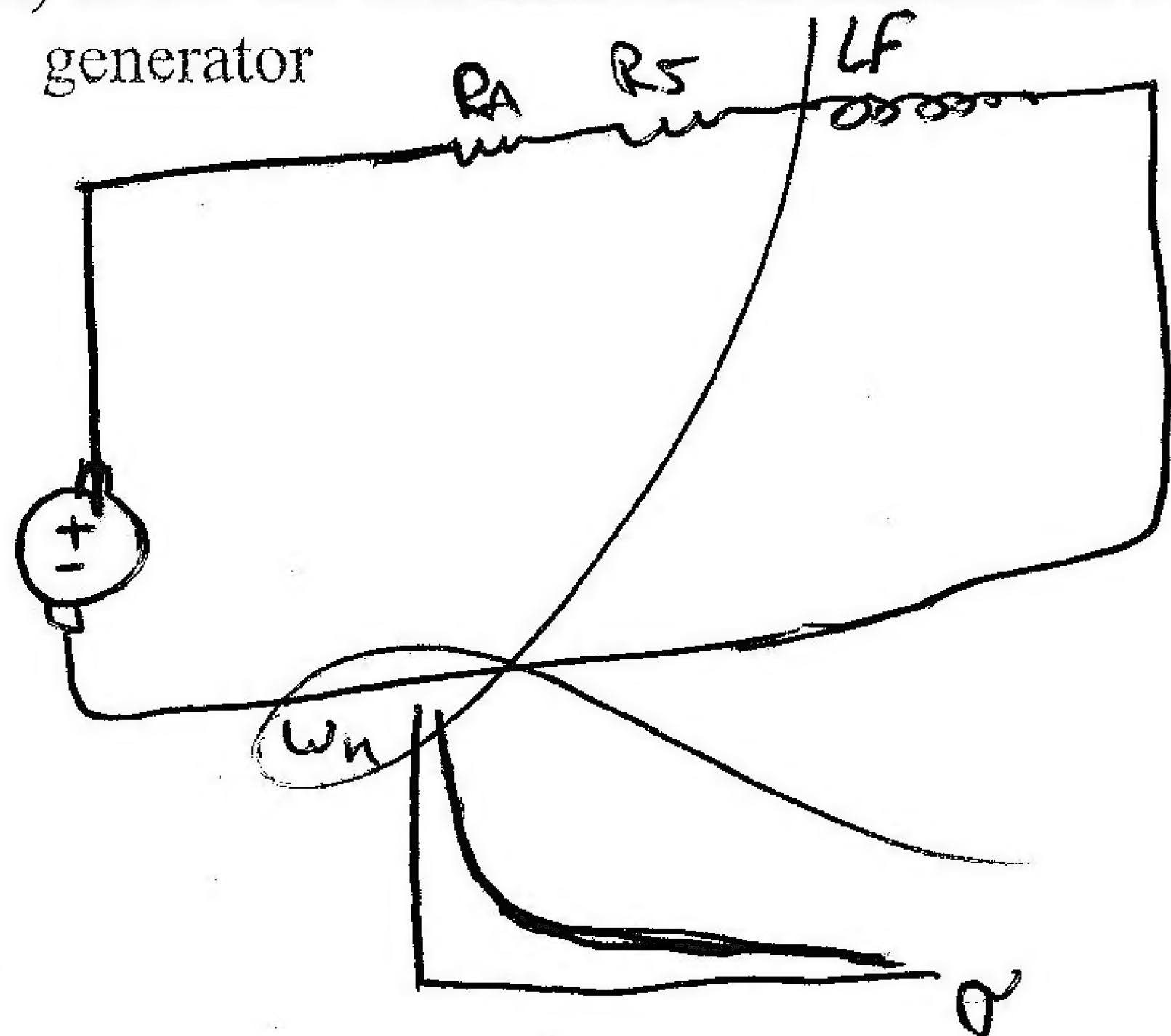a) Draw the terminal characteristics of series dc generator



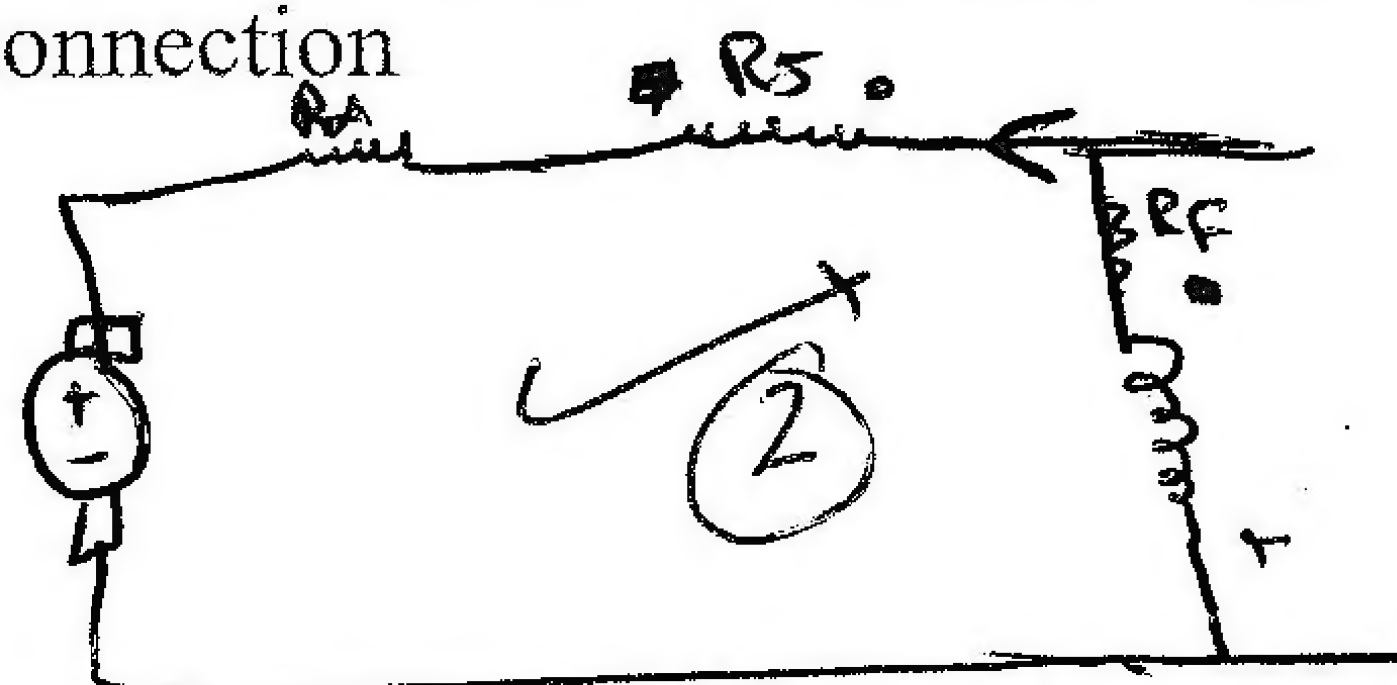
b) Draw the equivalent circuit of cumulative compound dc motor with long-shunt connection



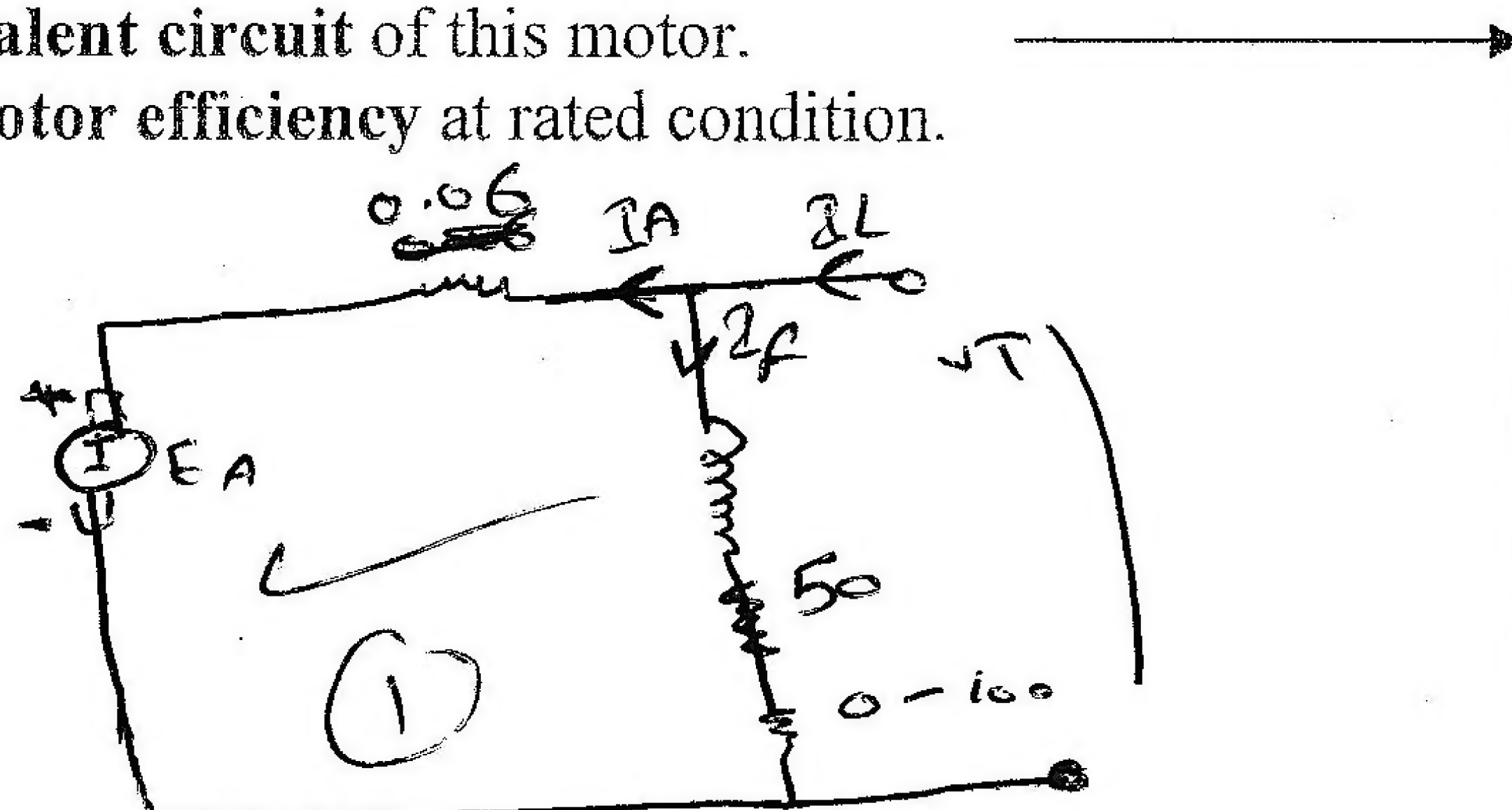Q4) (15 points) (4)

A 50 hp, 250V, 1200rpm shunt dc motor has an armature resistance of 0.06Ω and field resistance of 50Ω at which the field current is rated. The armature current is 170 A. The adjust resistance $R_{adj} = 0-100\Omega$.

- 1- Draw the equivalent circuit of this motor.
- 2- Calculate the motor efficiency at rated condition.



hp = 1

the motor efficiency = $\frac{V_m - V_{f1}}{V_{f1}} \times 100\%$
 $= \frac{250 - 239.8}{239.8} = 4.2\%$

$V_{f1} = \frac{250}{50} = 5A$
 $E_{a1} = 239.8V$

- 3- Calculate the maximum speed in rpm for constant rated armature current.

The maximum speed at $R_{adj} = 100$

$I_f = \frac{250}{150} = 1.66A$

$I_A = I_L - 1.66$
 $170 = I_L - 1.66 \Rightarrow I_L = 171.66A$

$E_A = V_T - I_A R_A = 250 - 170(0.06) = 250 - 10.2 = 239.8V$

$E_1 = E_2$

$E_{A1} = K\phi\omega_1 = E_{A2} = K\phi\omega_2$

$\frac{E_{A2}}{E_{A1}} = \frac{K\phi\omega_2}{K\phi\omega_1}$
 $\Rightarrow \omega_2 = \frac{E_{A2}\omega_1}{E_{A1}}$

$\frac{T_2}{T_1} = \frac{K\phi_2 I_{A2}}{K\phi_1 I_{A1}}$
 $\Rightarrow \frac{T_2}{T_1} = \frac{\phi_2 I_{A2}}{\phi_1 I_{A1}}$